

Design and Implementation of Clock Generation Circuits Using Monostable and Astable Configurations with LM741 and 555 Timer

Complex Engineering Activity



From

MUHAMMAD ZEESHAN	210711
MUHAMMAD ABDULLAH	210779
UMER ZAKI	211909

To

SIR MASHOOD AHMED

**DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING
FACULTY OF ENGINEERING
AIR UNIVERSITY, ISLAMABAD**

Abstract

This project focuses on the design and implementation of clock generation circuits using Monostable and Astable configurations with the LM741 operational amplifier and the 555 timer IC. Clock generation circuits are vital for providing precise timing signals in various electronic applications, including synchronization, data transfer, and control systems. We will develop two Monostable circuits: one utilizing the LM741 and another using the 555 timer, both designed to generate a 0.1-second pulse upon receiving a trigger. Additionally, we will create two Astable circuits: one using the LM741 to produce a 1kHz square wave and another with the 555 timer to generate a 1kHz square wave with a 60 percent duty cycle. The designs will be simulated using Proteus software to ensure accuracy and functionality and then constructed on Veroboard for practical validation. This project demonstrates the versatility and reliability of the LM741 and 555 timer ICs in generating precise timing signals for a range of electronic applications.

Table of Contents

Abstract	iii
Table of Contents	iv
List of Figures	vi
Chapter 1: Introduction	1
1.1 Background	1
1.2 Problem Statement	2
1.3 Objective	2
Chapter 2: Apparatus	3
2.1 Components	3
2.2 Components Explanation	5
Chapter 3: Calculation	9
3.1 Astable Multivibrator Design Using 555 Timer	9
3.1.1 Threshold Voltage V_{th} :	11
3.2 Equations for Astable Multivibrator Circuit Using Operational Amplifier	12
3.3 Monostable multivibrator using Operational Amplifier	13
Chapter 4: Software	16
4.1 Proteus Design Suite	16
4.2 Monostable Circuit Using LM741	16
4.2.1 Implementation	16
4.2.2 Output Waveform	17
4.2.3 Circuit Description	17
4.3 Monostable Circuit Using 555 Timer	18
4.3.1 Implementation	18
4.3.2 Output Waveform	18

4.3.3	Circuit Description	19
4.4	Astable Circuit Using LM741	19
4.4.1	Implementation	19
4.4.2	Output Waveform	20
4.4.3	Circuit Description	20
4.5	Astable Circuit Using 555 Timer	21
4.5.1	Implementation	21
4.5.2	Output Waveform	21
4.5.3	Circuit Description	22
Chapter 5:	Working	23
5.1	Monostable Multivibrator using LM741	23
5.1.1	Initial:	23
5.1.2	After Pulse:	23
5.2	Monostable Multivibrator using 555 Timer	23
5.3	Astable Multivibrator using LM741	24
5.4	Astable Multivibrator using 555 Timer	25
Chapter 6:	Conclusion	26

List of Figures

Figure 2.1	LM741	5
Figure 2.2	555 Timer	5
Figure 2.3	(a)Resistor symbol (b)Resistor	6
Figure 2.4	(a)capacitor (b)capacitor symbol	6
Figure 2.5	Push Button	7
Figure 2.6	Power Supply	7
Figure 2.7	Conecting Wire	8
Figure 2.8	Oscilloscope	8
Figure 4.1	Proteus Logo	16
Figure 4.2	Circuit Diagram of Monostable Circuit Using LM741	16
Figure 4.3	Output Waveform of Monostable Circuit Using LM741	17
Figure 4.4	Circuit Diagram of Monostable Circuit Using 555 Timer	18
Figure 4.5	Output Waveform of Monostable Circuit Using 555 Timer	18
Figure 4.6	Circuit Diagram of Astable Circuit Using LM741	20
Figure 4.7	Output Waveform of Astable Circuit Using LM741	20
Figure 4.8	Circuit Diagram of Astable Circuit Using 555 Timer	21
Figure 4.9	Output Waveform of Astable Circuit Using 555 Timer	22

Chapter 1

Introduction

1.1 Background

Timing circuits play a crucial role in electronics, facilitating the generation of precise timing signals essential for many applications. Among the various timing circuit configurations, monostable and astable multivibrators stand out for their versatility and utility. A monostable multivibrator, often called a one-shot circuit, generates a single pulse of predetermined duration in response to an external trigger. This feature finds applications in pulse shaping, time delay circuits, and pulse-width modulation.

Conversely, an astable multivibrator, a free-running oscillator, produces a continuous square wave output without needing external triggering. Astable circuits are commonly employed in applications requiring constant timing signals, such as clock generators, tone generation, and frequency modulation. Understanding the principles underlying the design and operation of monostable and astable circuits is essential for engineers and enthusiasts, as they form the backbone of many electronic systems.

In this project, we explore the design and implementation of monostable and astable circuits using two distinct integrated circuit components: the LM741 operational amplifier and the 555 timer IC. Both components offer unique advantages and capabilities, making them widely used in analogue and timing circuit designs. Through practical experimentation and analysis, we aim to deepen our understanding of these circuits' functionality, performance characteristics, and practical considerations in generating precise timing signals for various electronic applications.

1.2 Problem Statement

You have to give a design of clock generation circuits using Monostable and Astable circuits:

1. Generate a 0.1-second pulse after trigger by designing a Monostable circuit using LM741.
2. Generate a 0.1-second pulse after trigger by designing a Monostable circuit using a 555 timer.
3. Generate a 1kHz square wave by designing an Astable circuit using LM741.
4. Generate a 1kHz square wave with a 60% dutycycle by designing an Astable circuit using a 555 timer.

1.3 Objective

This project aims to design clock generation circuits using monostable and astable configurations. Specifically, the project aims to achieve the following objectives:

- Design a monostable circuit using the LM741 operational amplifier to generate a 0.1-second pulse after the trigger.
- Design a monostable circuit using the 555 timer IC to generate a 0.1-second pulse after the trigger.
- Design an astable circuit using the LM741 operational amplifier to generate a 1kHz square wave.
- Design an astable circuit using the 555 timer IC to generate a 1kHz square wave with a 60% duty cycle.

Chapter 2

Apparatus

2.1 Components

Monostable Circuit Using LM741

Objective: Generate a 0.1-second pulse after trigger.

Components :

LM741 Operational Amplifier

Resistors

Capacitors

Trigger switch (push button)

Power supply($\pm 15V$ for LM741)

Oscilloscope (for testing output waveform)

Monostable Circuit Using 555 Timer

Objective: Generate a 0.1-second pulse after trigger.

Components :

555 Timer IC

Resistors (various values, including one for the timing configuration)

Capacitors (various values, including one for the timing configuration)

Trigger switch (push button)

Power supply(5V or 9V for 555 Timer)

Oscilloscope (for testing output waveform)

Astable Circuit Using LM741

Objective: Generate a 1kHz square wave.

Components :

- LM741 Operational Amplifier
- Resistors (for frequency setting)
- Capacitors (for frequency setting)
- Power supply($\pm 15V$ for LM741)
- Oscilloscope (for testing output waveform)
- Connecting wires

Astable Circuit Using 555 Timer

Objective: Generate a 1kHz square wave with a 60

Components :

- 555 Timer IC
- Resistors
- Capacitors)
- Power supply($5V$ for 555 Timer)
- Oscilloscope (for testing output waveform)
- Connecting wires

2.2 Components Explanation

- **LM741 Operational Amplifier:** An operational amplifier used in analog circuits for a variety of applications including signal amplification, filtering, and waveform generation. It requires a dual power supply ($\pm 15V$) for proper operation.



Figure 2.1: LM741

- **555 Timer IC:** A highly versatile IC used in timer, delay, pulse generation, and oscillator applications. It operates on a single power supply, typically 5V or 9V.



Figure 2.2: 555 Timer

- **Resistors:** Used to control current flow, set timing intervals, and define the operational parameters of the circuits. Specific values will be chosen based on the desired pulse duration and frequency.



Figure 2.3: (a)Resistor symbol (b)Resistor

- **Capacitors:** Store and release electrical energy, used in timing circuits to set the duration of pulses and oscillation frequency. The values of capacitors, in combination with resistors, determine the timing characteristics.

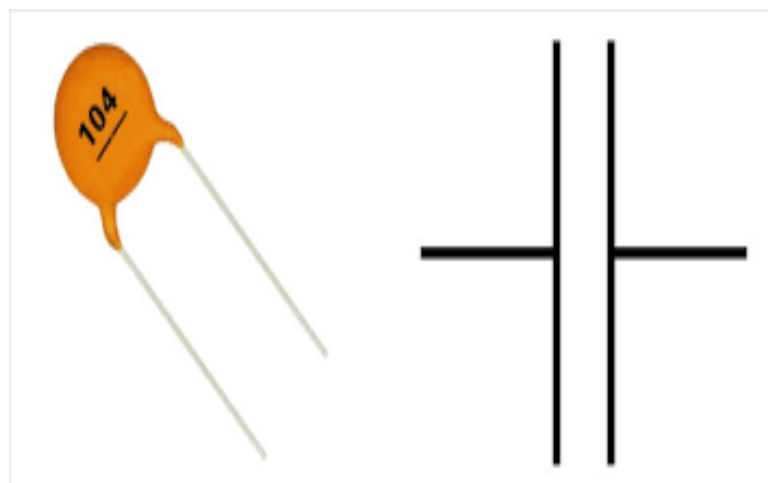


Figure 2.4: (a)capacitor (b)capacitor symbol

- **Trigger Switch (Push Button):** A momentary switch used to provide an external trigger signal to the Monostable circuits. Pressing the button initiates the timing pulse.

Design and Implementation of Clock Generation Circuits Using Monostable and Astable Configurations with LM741 and 555 Timer

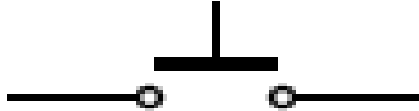


Figure 2.5: Push Button

- **Power Supply:** Provides the necessary voltage for the operation of the LM741 and 555 timer circuits. LM741 requires a dual $\pm 15V$ supply, while the 555 timer typically uses a single 5V or 9V supply.



Figure 2.6: Power Supply

- **Breadboard or Veroboard:** Breadboard is used for prototyping and testing circuit designs quickly without soldering. Veroboard (stripboard) is used for the permanent construction of the circuits by soldering components.

- **Connecting Wires:** Used to make electrical connections between components on the breadboard or veroboard.



Figure 2.7: Connecting Wire

- **Oscilloscope:** A test instrument that allows observation of varying signal voltages, is used to visualize the output waveform of the Astable circuits to verify the correct frequency and duty cycle.

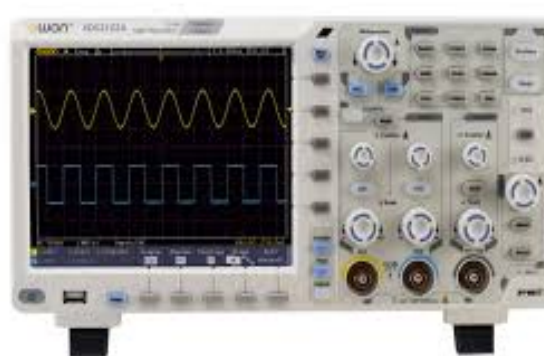


Figure 2.8: Oscilloscope

Chapter 3

Calculation

3.1 Astable Multivibrator Design Using 555 Timer

To design an astable multivibrator using the 555 timer with a target frequency of 1 kHz, we perform the following calculations:

1. Determine the Period T from the Frequency f

$$f = 1000 \text{ Hz}$$

$$T = \frac{1}{f} \tag{3.1}$$

$$T = \frac{1}{1000 \text{ Hz}} = 0.001 \text{ seconds} = 1 \text{ ms}$$

2. Express the Time Period T in Terms of R_a , R_b , and C

$$T = 0.693 \times C \times (R_a + 2R_b) \tag{3.2}$$

3. Choose a Practical Capacitor Value C

$$C = 1 \mu F$$

4. Calculate the Required Resistance Using the Time Period T

$$0.001 = 0.693 \times 1 \times 10^{-6} \times (R_a + 2R_b)$$

$$R_a + 2R_b = \frac{0.001}{0.693 \times 1 \times 10^{-6}}$$

$$R_a + 2R_b = \frac{0.001}{6.93 \times 10^{-9}}$$

$$R_a + 2R_b = 1449.275 \Omega$$

$$R_a = 1449.27 - 2R_b \quad (3.3)$$

5. Calculate the Duty Cycle D

$$D = \frac{R_a + R_b}{R_a + 2R_b} \quad (3.4)$$

6. Choose Values for R_a and R_b

Assume a duty cycle around 50%. For a 50% duty cycle:

$$D = 0.6$$

$$0.6 = \frac{R_a + R_b}{R_a + 2R_b}$$

$$0.6 = \frac{1449.275 - 2R_b + R_b}{1449.275 - 2R_b + 2R_b}$$

$$869.565 = 1449.275 - R_b$$

$$R_b = 1449.275 - 869.565$$

$$R_b = 579.709 \Omega$$

Substitute $R_b = 579.709$ into the earlier equation:

$$R_a = 1449.275 - 2(579.709) \Omega$$

$$R_a = 1449.275 - 1159.42 \Omega$$

$$R_a = 289.855 \Omega$$

Thus:

$$R_a = 289.855 \Omega \quad (3.5)$$

Design and Implementation of Clock Generation Circuits Using Monostable and Astable Configurations with LM741 and 555 Timer

$$R_b = 579.709 \Omega \quad (3.6)$$

3.1.1 Threshold Voltage V_{th} :

$$V_{th} = \frac{2}{3}V_{cc} \quad (3.7)$$

$$V = IR \quad (3.8)$$

$$5 - 3.33 = (3.33 \times 10^{-3})R$$

$$R = \frac{5 - 3.33}{3.33 \times 10^{-3}}$$

$$R = \frac{1.67}{3.33 \times 10^{-3}}$$

$$R = (501.5 \times 10^3)$$

$$R = 501.5 k\Omega \quad (3.9)$$

Monostable Multivibrator Design Using 555 Timer

1. Determine Pulse Width (T) from External Components

The pulse width, T , is determined by the timing resistor (R) and timing capacitor (C) according to the formula:

$$T = 1.1 \times R \times C$$

Choose a desired pulse width (T) for your application.

2. Choose a Practical Capacitor Value (C)

Select a suitable capacitor value based on the desired pulse width and the timing resistor.

Rearrange the formula to solve for C :

$$C = \frac{T}{1.1 \times R}$$

For example, if $C = 10 \times 10^{-6})k\Omega$ and $T = 0.1$ s:

$$R = \frac{0.1}{1.1 \times 10^{-6}} = 90909.0909 \Omega$$

3.2 Equations for Astable Multivibrator Circuit Using Operational Amplifier

1. Frequency (f) and Period (T) Relationship

The frequency (f) and period (T) are related by:

$$f = \frac{1}{T}$$

2. Feedback Factor (B) Equation

The feedback factor (B) is calculated as:

$$B = \frac{R_1}{R_1 + R_2}$$

When $R_1 = R_2$, we have:

$$B = \frac{1}{2}$$

3. Duty Cycle (D) and Feedback Factor (B) Relationship

The duty cycle (D) and feedback factor (B) are related by:

$$D = \frac{1 - B}{1 + B}$$

4. Period (T) Equation

The period (T) of the astable multivibrator circuit is given by:

$$T = 2RC \cdot \ln \left(\frac{1 + B}{1 - B} \right)$$

$$T = 1 \text{ ms}$$

$$R_1 = R_2$$

$$T = 2RC \cdot \ln(3)$$

$$C = 0.5 \times 10^{-6}$$

$$1 \times 10^{-3} = 2R(0.5 \times 10^{-6}) \cdot \ln(3)$$

$$R = 1 \text{ k}\Omega$$

3.3 Monostable multivibrator using Operational Amplifier

1. Voltage Divider:

$$B = \frac{R_2}{R_1 + R_2}$$

2. Input Voltage:

$$V_{in} = B \cdot V_{sat}$$

3. Time Constant:

$$T = RC \ln \left(1 + \frac{R2}{R1} \right)$$

Given values:

$$R1 = 10\text{k}\Omega$$

$$R2 = 10\text{k}\Omega$$

$$C = 10\mu\text{F} = 10 \times 10^{-6}\text{F}$$

$$T = 0.1\text{s}$$

The time constant equation is:

$$T = RC \ln \left(1 + \frac{R2}{R1} \right)$$

First, calculate the logarithmic term:

$$\frac{R2}{R1} = \frac{10\text{k}\Omega}{10\text{k}\Omega} = 1$$

$$\ln \left(1 + \frac{R2}{R1} \right) = \ln(1 + 1) = \ln(2)$$

Using the value of $\ln(2)$:

$$\ln(2) \approx 0.693$$

Substitute into the time constant equation:

$$T = RC \cdot 0.693$$

Design and Implementation of Clock Generation Circuits Using Monostable and Astable Configurations with LM741 and 555 Timer

Now, substitute $T = 0.1\text{s}$ and $C = 10\mu\text{F}$:

$$0.1 = R \cdot 10 \times 10^{-6} \cdot 0.693$$

Solve for R :

$$0.1 = R \cdot 6.93 \times 10^{-6}$$

$$R = \frac{0.1}{6.93 \times 10^{-6}}$$

$$R = 14.43\text{k}\Omega \tag{3.10}$$

Therefore, the total resistance R required to achieve a time constant T of 0.1 seconds with a capacitance of $10\mu\text{F}$ is approximately $14.43\text{k}\Omega$.

Chapter 4

Software

4.1 Proteus Design Suite

Proteus is a powerful simulation software used for electronic circuit design and simulation. It provides a comprehensive environment for designing, testing, and debugging circuits before they are implemented in hardware.



Figure 4.1: Proteus Logo

4.2 Monostable Circuit Using LM741

4.2.1 Implementation

Here is the simulated circuit using Proteus:

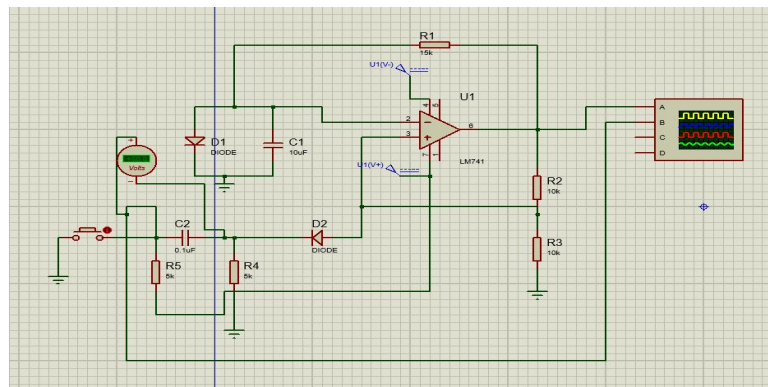


Figure 4.2: Circuit Diagram of Monostable Circuit Using LM741

Design and Implementation of Clock Generation Circuits Using Monostable and Astable Configurations with LM741 and 555 Timer

4.2.2 Output Waveform

The output waveform of the Monostable circuit generated by Proteus is shown below:

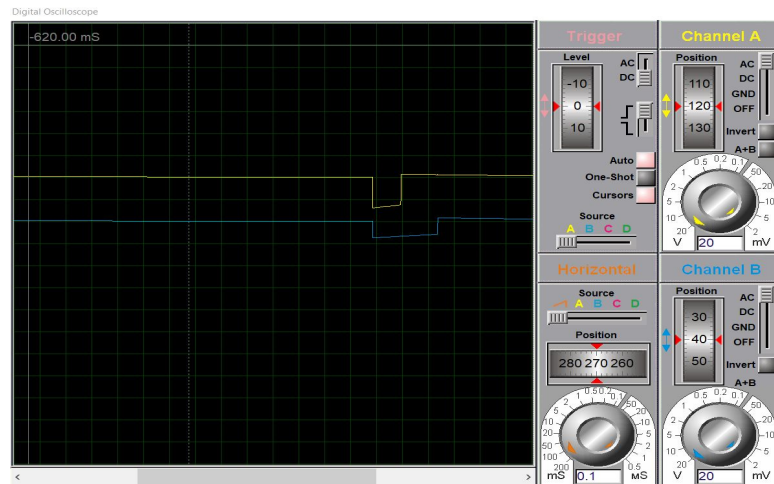


Figure 4.3: Output Waveform of Monostable Circuit Using LM741

4.2.3 Circuit Description

Power Supply:

- Connect the V_{CC} (15V) to pin 7 and V_{EE} (-15V) to pin 4.

Feedback Network:

- Connect a resistor R between the output (pin 6) and the inverting input (pin 2).

Timing Network:

- Connect a capacitor C and diode in parallel between the inverting input (pin 2) and ground.

Triggering:

- Connect the non-inverting input (pin 3) to a trigger pulse source(push button) through a suitable coupling capacitor and diode for only one directional output change.

Initial Conditions:

- Ensure that the capacitor C is initially uncharged.

4.3 Monostable Circuit Using 555 Timer

4.3.1 Implementation

Here is the simulated circuit using Proteus:

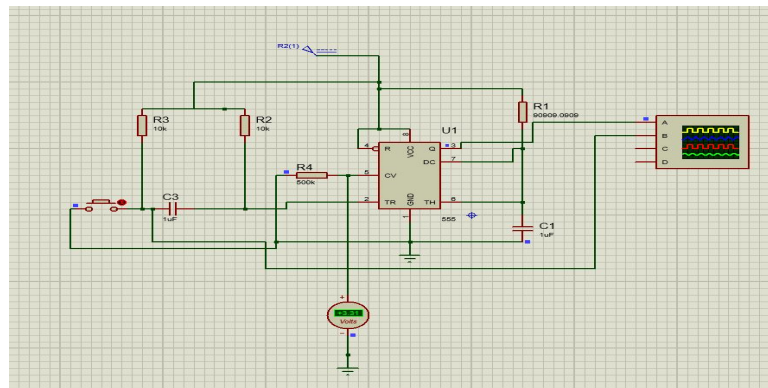


Figure 4.4: Circuit Diagram of Monostable Circuit Using 555 Timer

4.3.2 Output Waveform

The output waveform of the Monostable circuit generated by Proteus is shown below:

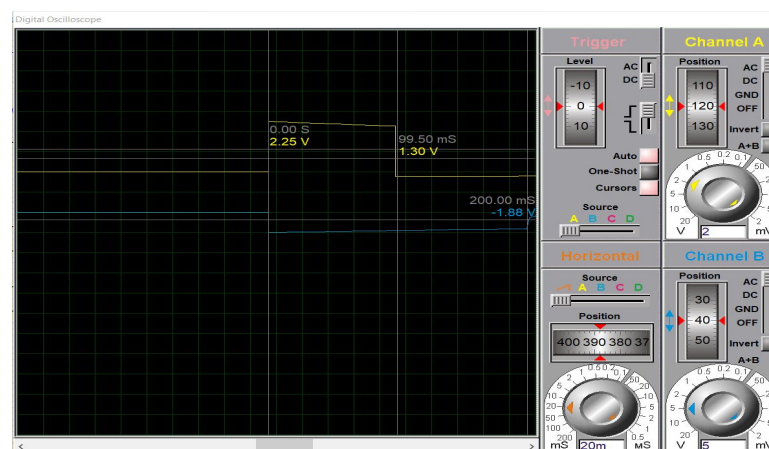


Figure 4.5: Output Waveform of Monostable Circuit Using 555 Timer

4.3.3 Circuit Description

Power Supply:

- Connect the positive supply voltage (V_{CC}) to pin 8 (Vcc).
- Connect the ground (0V) to pin 1 (GND).

Feedback Network:

- Connect a resistor (R) between the output (pin 3) and the discharge pin (pin 7).

Timing Network:

- Connect a capacitor (C) between the threshold pin (pin 6) and the trigger pin (pin 2).

Triggering:

- Connect the trigger pin (pin 2) to a switch through a suitable coupling capacitor with 2 pullup resistors.

Initial Conditions:

- Ensure that the capacitor (C) is initially uncharged.

4.4 Astable Circuit Using LM741

4.4.1 Implementation

Here is the simulated circuit using Proteus:

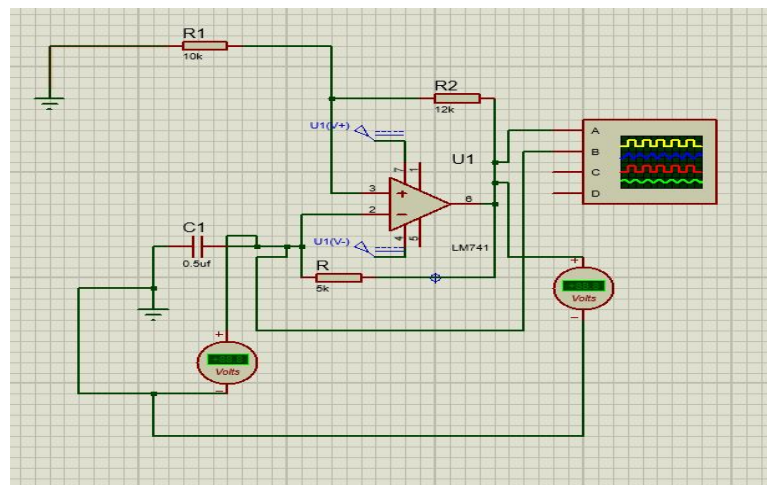


Figure 4.6: Circuit Diagram of Astable Circuit Using LM741

4.4.2 Output Waveform

The output waveform of the Astable circuit generated by Proteus is shown below:

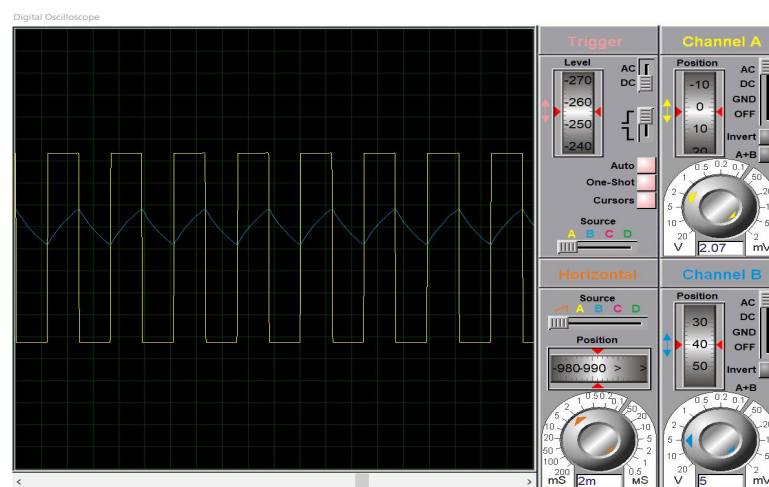


Figure 4.7: Output Waveform of Astable Circuit Using LM741

4.4.3 Circuit Description

Power Supply:

- Connect the V_{CC} (15 V) to pin 7.
- Connect the V_{CC} (-15 V) to pin 4.

Design and Implementation of Clock Generation Circuits Using Monostable and Astable Configurations with LM741 and 555 Timer

Feedback Network:

- Connect a resistor R between pin (pin 6) and the pin (pin 3).
- Also, Connect a resistor R between pin (pin 6) and the pin (pin 2).

Timing Network:

- Connect a capacitor C between the inverting input (pin 2) and ground.

Initial Conditions:

- Ensure that the capacitor C is initially uncharged.

4.5 Astable Circuit Using 555 Timer

4.5.1 Implementation

Here is the simulated circuit using Proteus:

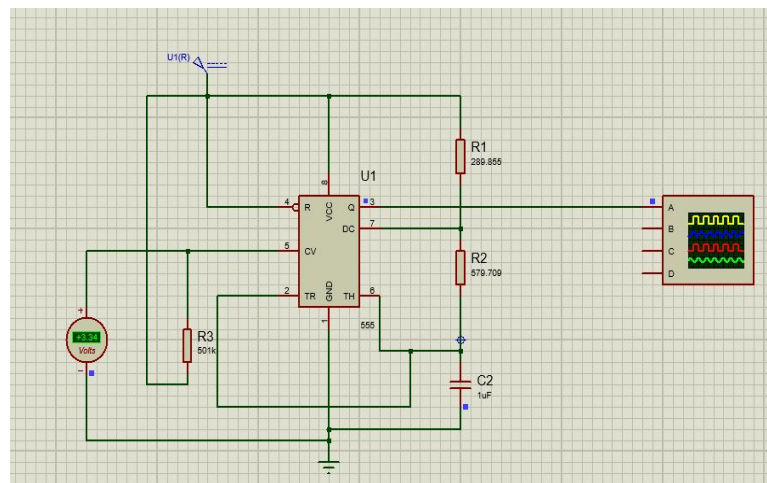


Figure 4.8: Circuit Diagram of Astable Circuit Using 555 Timer

4.5.2 Output Waveform

The output waveform of the Astable circuit generated by Proteus is shown below:

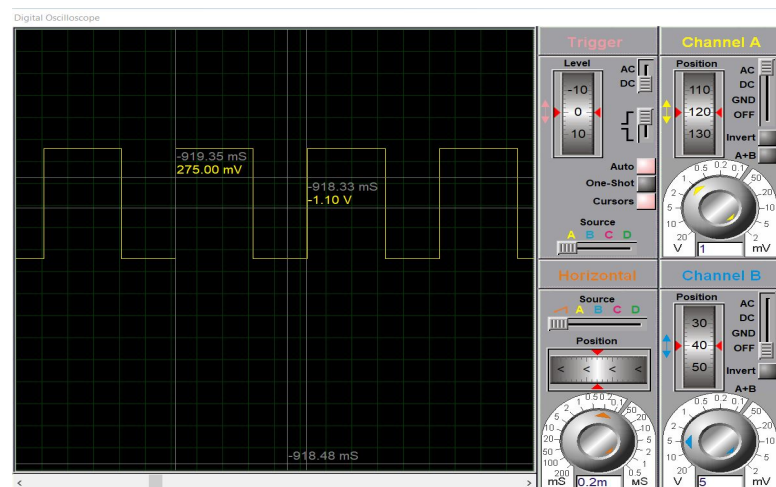


Figure 4.9: Output Waveform of Astable Circuit Using 555 Timer

4.5.3 Circuit Description

Power Supply:

- Connect the positive supply voltage (V_{CC}) to pin 8.
- Connect the ground (0V) to pin 1.

Feedback Network:

- Connect a resistor (R_1) between pins 7 (Discharge) and 8 (VCC).
- Connect pins 2 (Trigger) and 6 (Threshold).
- Connect another resistor (R_2) between pins 7 (Discharge) and 6 (Threshold/Trigger).

Timing Network:

- Connect a capacitor (C) between pins 6 (Threshold/Trigger) and 1 (Ground).

Initial Conditions:

- The capacitor C is initially discharged.

Chapter 5

Working

5.1 Monostable Multivibrator using LM741

Working Principle: When the pulse is given then the output goes into an unstable state.

5.1.1 Initial:

1. Initially, the capacitor (C) is discharged, and the output at pin 6 is low.
2. The output is in its initial state.
3. Diode will be forward biased and the voltage at the capacitor will be the forward voltage across the diode.
4. The output voltage will be the forward voltage across the diode.

5.1.2 After Pulse:

1. The output goes to the unstable state.
2. Diode will become reverse biased and the capacitor starts charging at negative saturation voltage
3. The diode attached to a capacitor is to eliminate the positive pulse.
4. The two resistors pull up and pull down across the capacitor to provide the potential difference across the capacitor to give the trigger.

5.2 Monostable Multivibrator using 555 Timer

Working Principle:

1. Initially, the capacitor (C) is discharged, and the output at pin 3 is low.

2. When a trigger input is applied to pin 2 (Trigger), the capacitor starts charging through resistor R connected between pins 7 (Discharge) and 8 (VCC).
3. The voltage across the capacitor rises.
4. When the voltage across the capacitor reaches $\frac{2}{3}$ of V_{CC} , the output switches to high for a duration determined by the values of R and C .
5. The capacitor then discharges through R .
6. The output returns to a low state, and the circuit waits for the next trigger pulse.

5.3 Astable Multivibrator using LM741

Output continuously changes its state. The opamp is used as positive feedback so this circuit is known as Schmitt trigger.

Working Principle:

1. Initially, the capacitor (C) is charged, and the output at pin 6 is high.
2. When the capacitor voltage becomes greater than the output voltage the output changes its state to negative voltage.
3. This is because there is feedback from the output to the input using a capacitor and resistor.
4. The capacitor starts discharging through resistors.
5. When the voltage across the capacitor reaches the voltage that is below the input then the opamp changes its output state.
6. The capacitor discharges through resistor R_2 .
7. The cycle repeats, resulting in a continuous square wave output.

5.4 Astable Multivibrator using 555 Timer

Working Principle:

1. Initially, the capacitor (C) is discharged, and the output at pin 3 is low.
2. The capacitor starts charging through resistors R_1 and R_2 connected between pins 7 (Discharge) and 8 (VCC).
3. When the voltage across the capacitor reaches $\frac{2}{3}$ of V_{CC} , the output switches to high.
4. The capacitor now discharges through R_2 .
5. When the voltage across the capacitor falls to $\frac{1}{3}$ of V_{CC} , the output switches back to low.
6. The cycle repeats, resulting in a continuous square wave output.

Chapter 6

Conclusion

In conclusion, this project successfully demonstrated the design and implementation of clock generation circuits using the LM741 operational amplifier and the 555 timer IC. Through the development of Monostable and Astable configurations, we achieved precise timing signals vital for synchronization, and data transfer, and creating delays in various applications.

These circuits offer versatile solutions for a wide range of electronic systems. In digital communication systems, they ensure accurate data transmission and reception by providing precise timing signals.

Furthermore, the seamless integration of simulation using Proteus software and practical validation on Veroboard ensured the functionality and accuracy of the designed circuits. This approach not only validated the effectiveness of the LM741 and 555 timer ICs in clock generation but also showcased a robust development methodology applicable to diverse electronic projects.